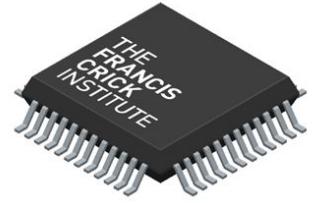



Microcontrollers (2022)

Session 3

Pulse Width Modulation (PWM)




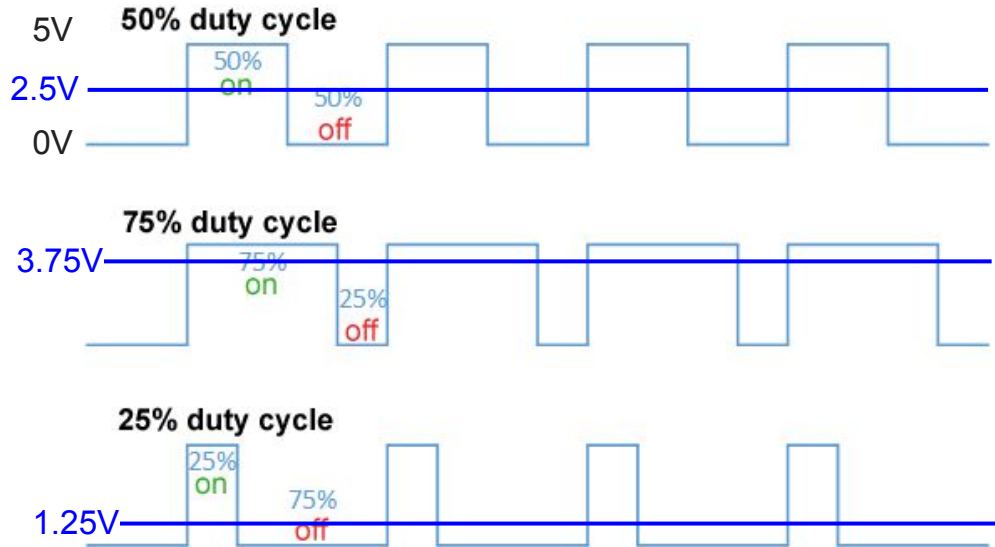The average value of **voltage** fed to the **load** is controlled by turning the switch between supply and load on and off at a **fast rate**.



That is what we use to perform gradual control of actuators such as DC motors, Servo motors, Brightness levels on LEDs ...

Pulse Width Modulation (PWM)

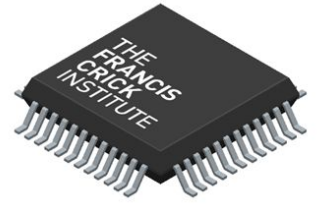

There are only certain pins that can do PWM

In the Arduino environment, the function to control PWM pins is called `analogWrite(Pin_number, dutyCycle)` (duty cycle has 8 bits and ranges 0-255 values)



In ESP32...

The `ledcWrite(Pin_number, dutyCycle)` is usually the function used in the ESP32 context.


Or downloading the ESP32_analogWrite library

https://github.com/erropix/ESP32_AnalogWrite

Pulse Width Modulation (PWM)

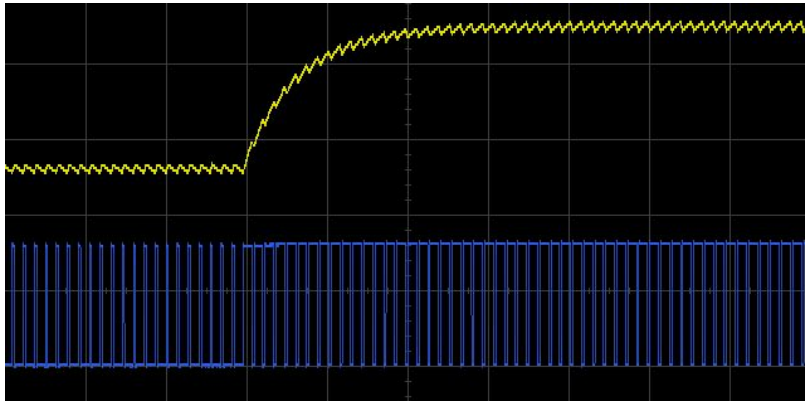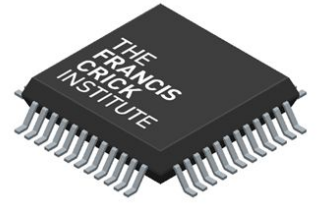


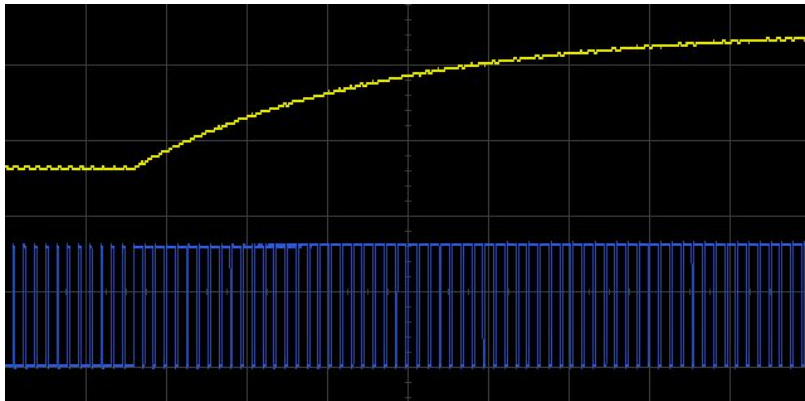PWM Filtered by 1K Resistor & 10 μ F Capacitor






PWM Filtered by 1K Resistor & 47 μ F Capacitor

PWM Audio

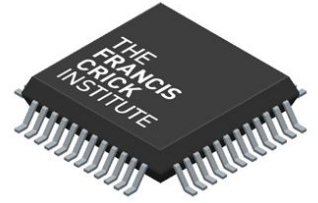


- <https://github.com/lbernstone/Tone32>
- <https://www.xtronical.com/the-dacaudio-library-download-and-installation/>

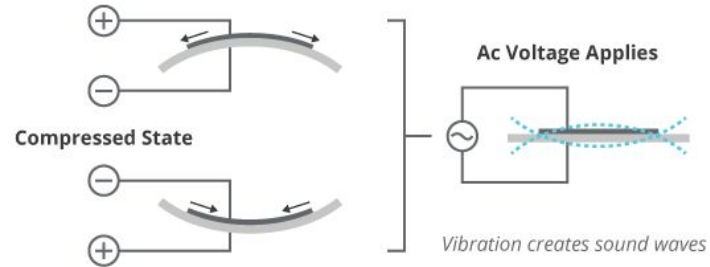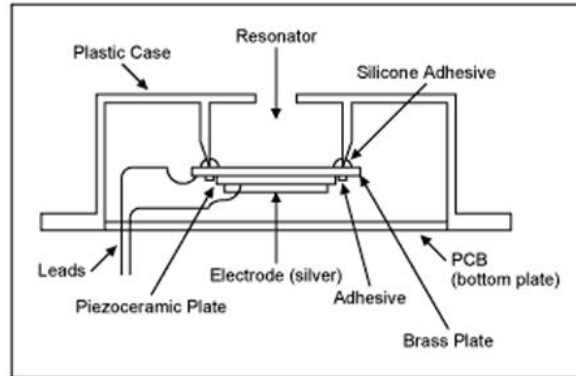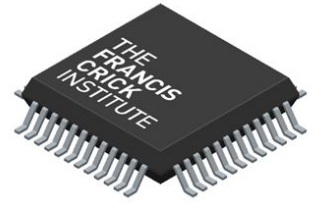Pulse Width Modulation (PWM): Sound examples




File->Examples->06.Sensors->Knock

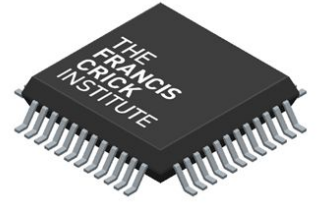
For some applications 20 or 40 mA is enough...



... for example to blink an LED:

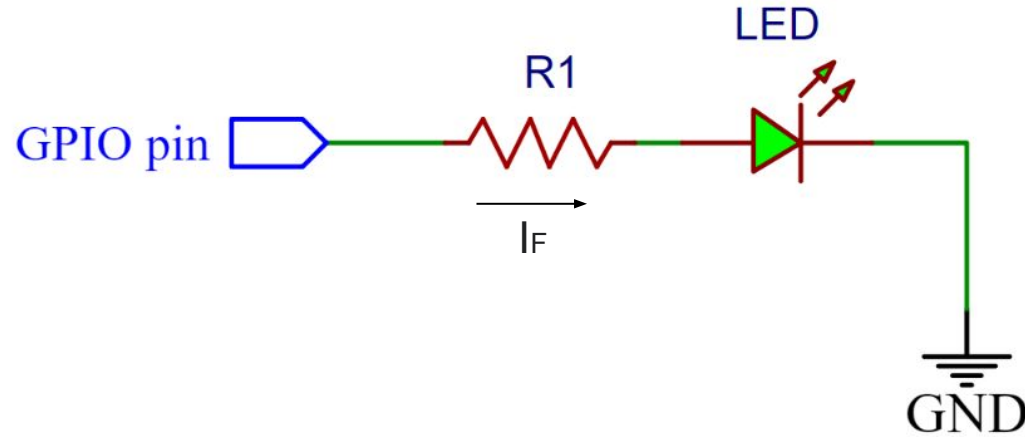


How to commute a higher power ?

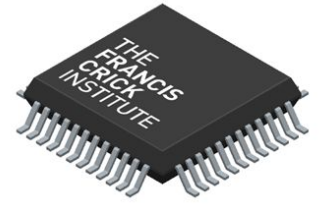


We have **current** and **voltage** controlled devices:

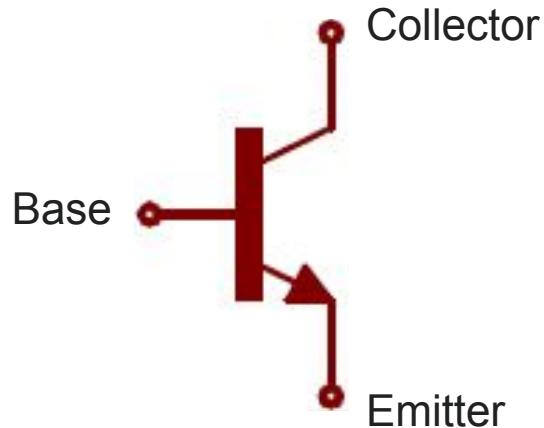
Current controlled devices:
BJT Transistors



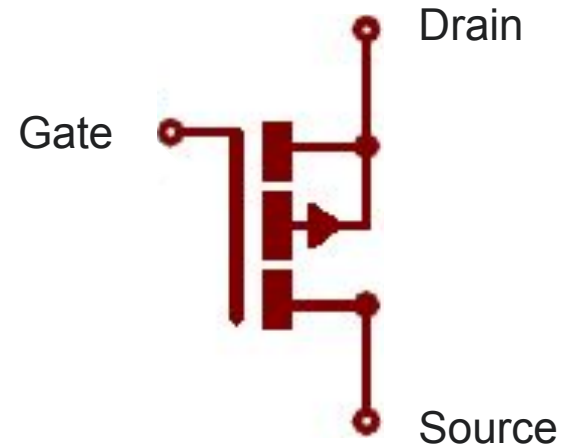
Voltage controlled devices:
FET Transistors



How to commute a higher power ?

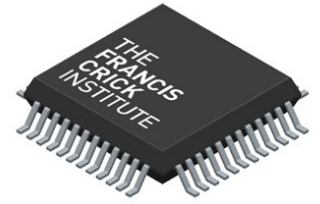

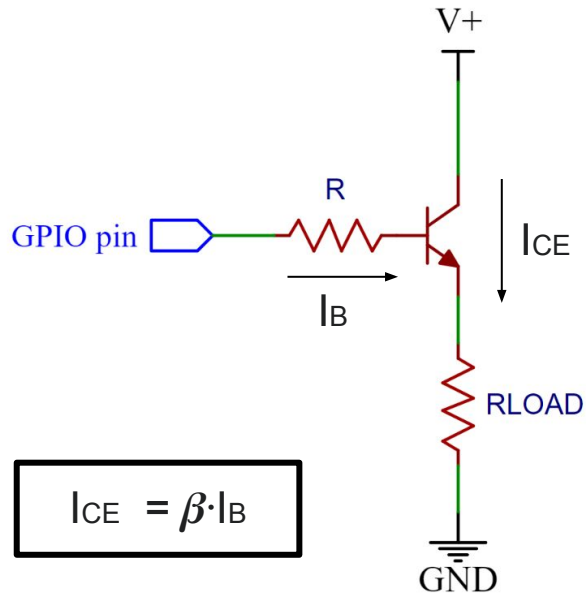
Current controlled devices: **BJT**
Transistors (“Intermediate power”)



$$I_{CE} = \beta \cdot I_B$$


β can be 50, 100 or more

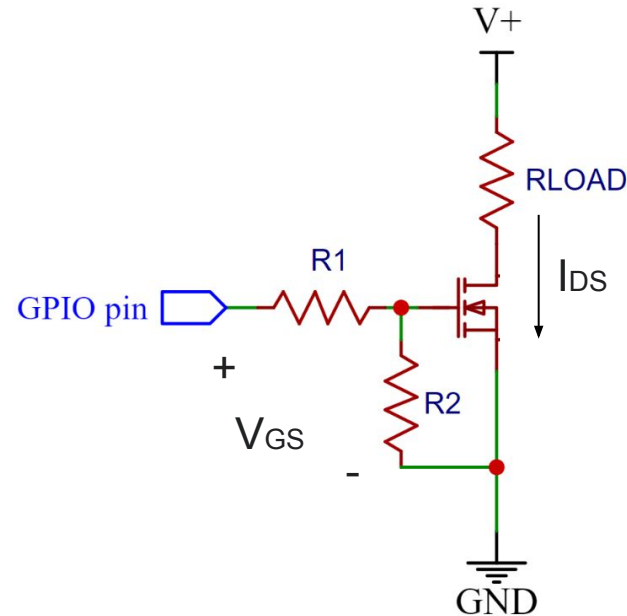Voltage controlled devices:
FET Transistors (“Higher power”)





R_{LOAD} will be a valve, LED ...


Darlington array

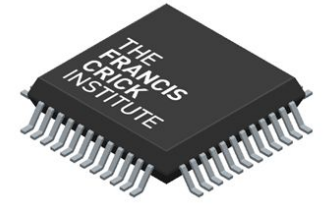


Cascade of two BJT Transistors

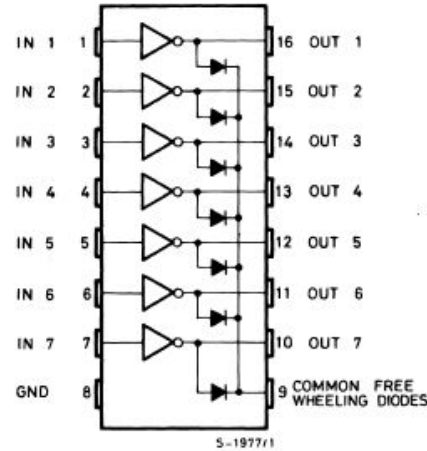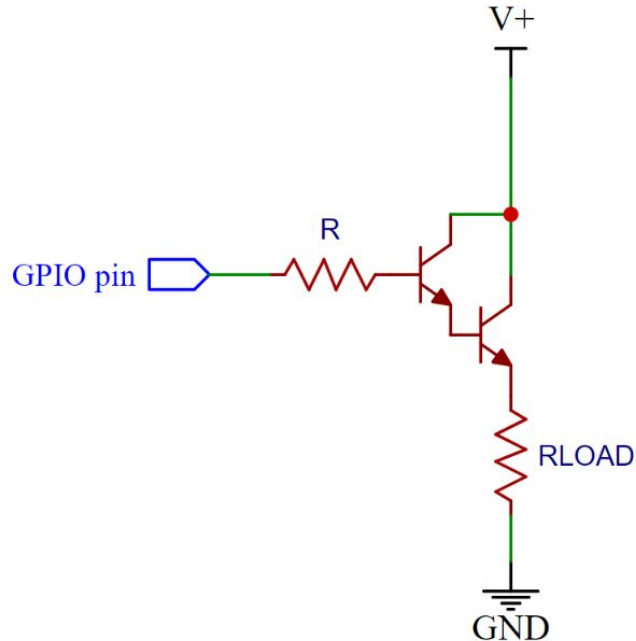

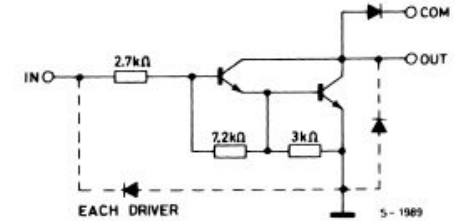
100 mA per channel at 3.3V
140 mA per channel at 5V




ULN2003 (each driver)

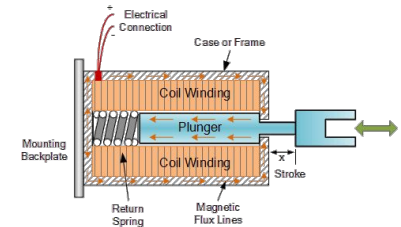





Valve control (Example 302)

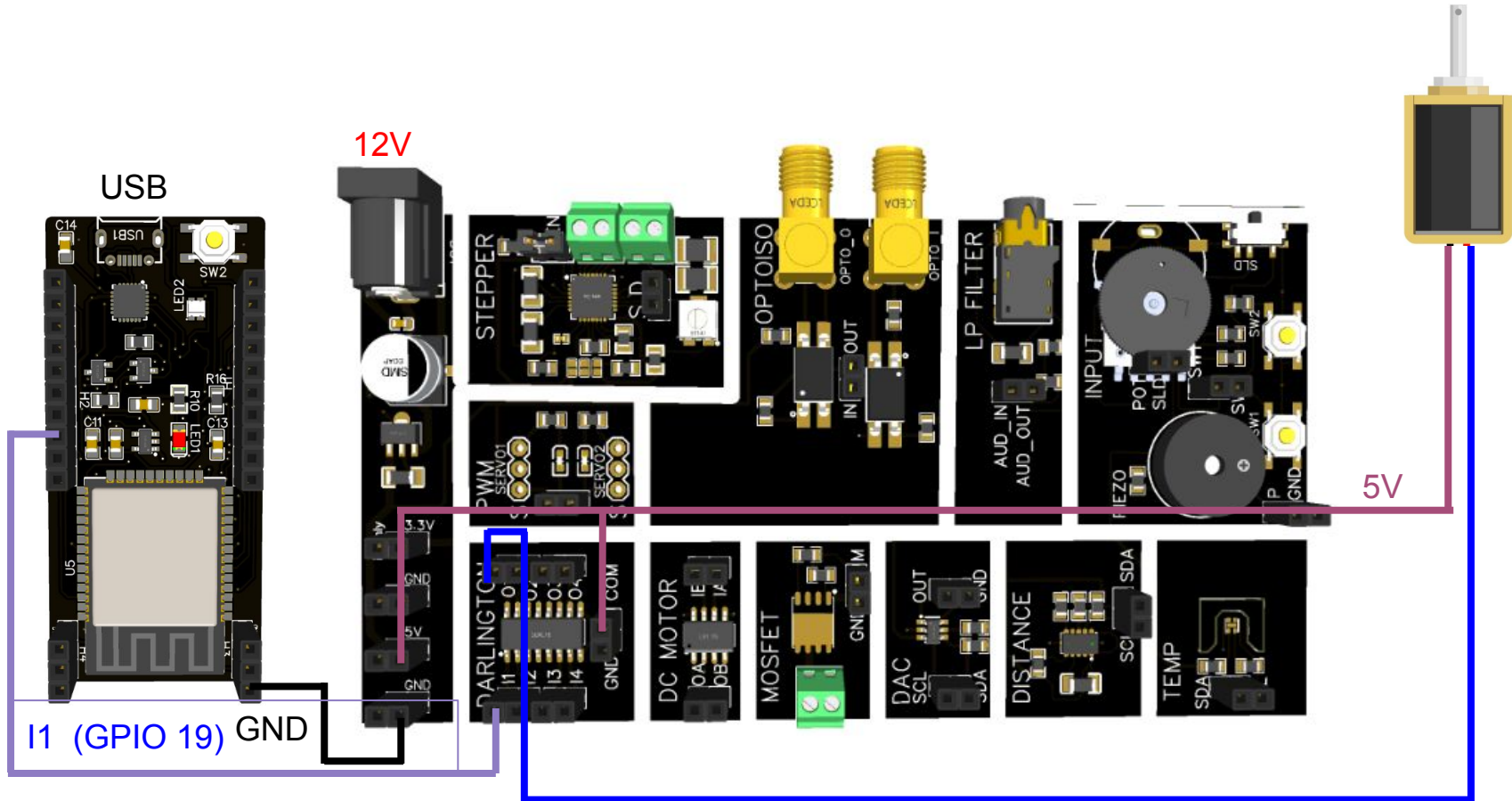


How to control DC motors: H-bridge

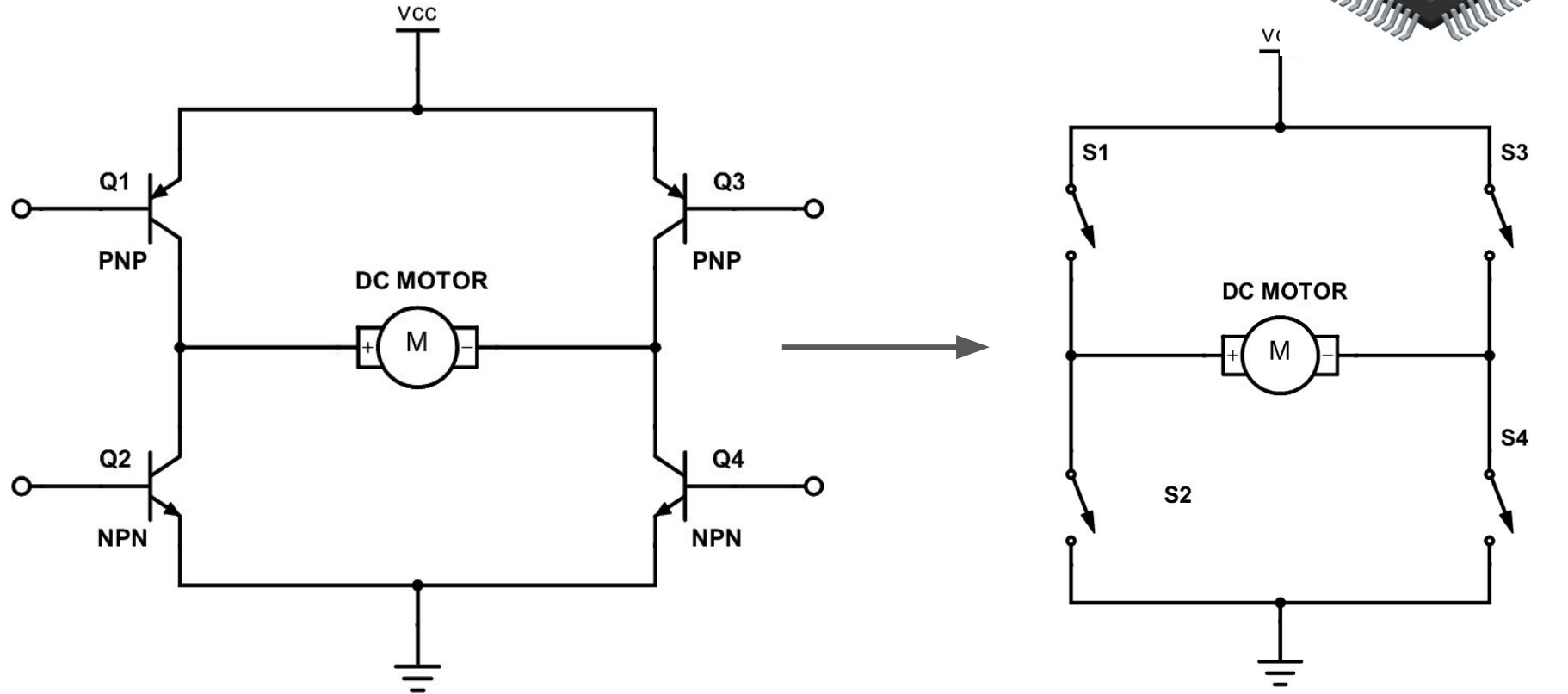

How to control DC motors: H-bridge

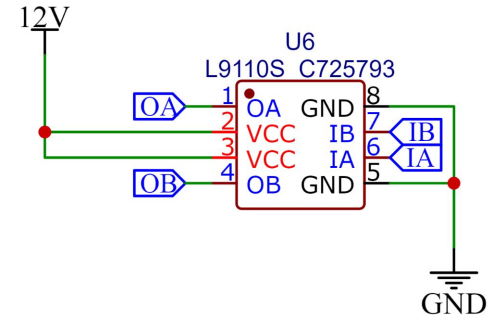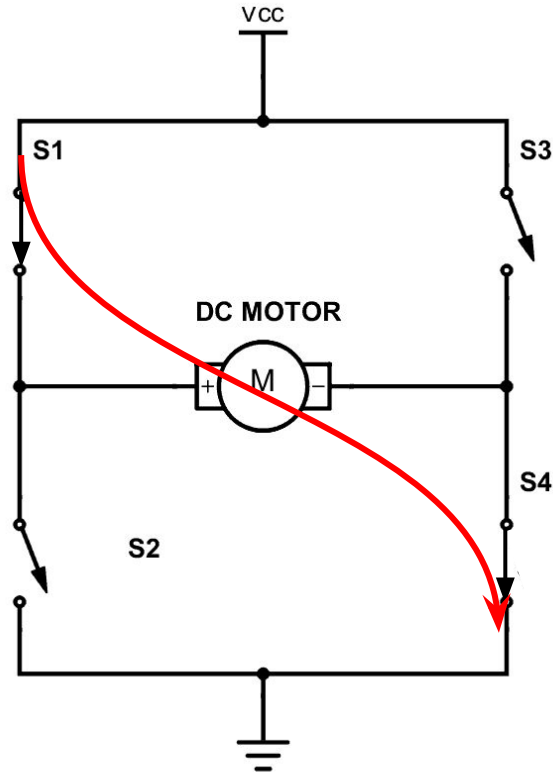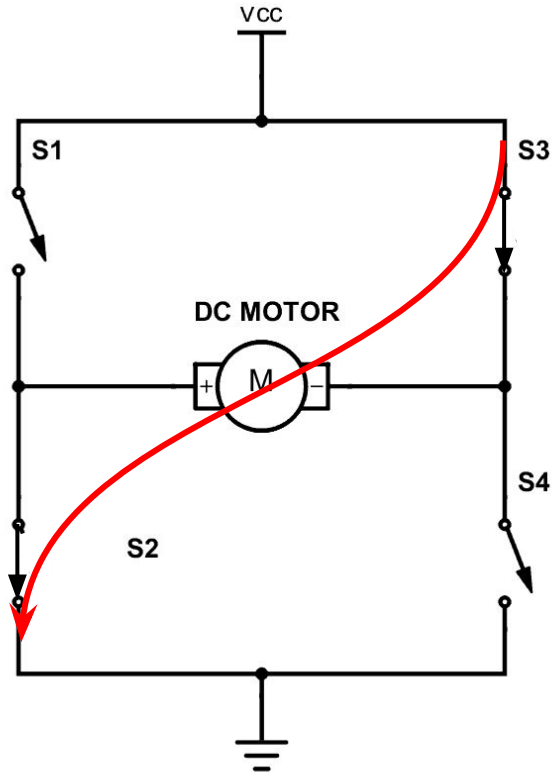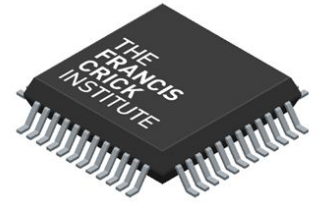

Making if/else structures more compact

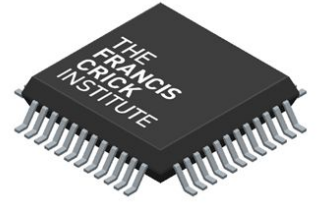

```
switch (var)
```

```
{
```

```
  case 1:
```

```
    // statements
```

```
    break;
```

```
  case 2:
```

```
    // statements
```

```
    break;
```

```
  case n:
```

```
    // statements
```

```
    break;
```

```
  default:
```

```
    // statements
```


```
    break;
```

```
}
```




var value

Equivalent to else (for any other condition)


IA & IB (GPIO 18 & 19)

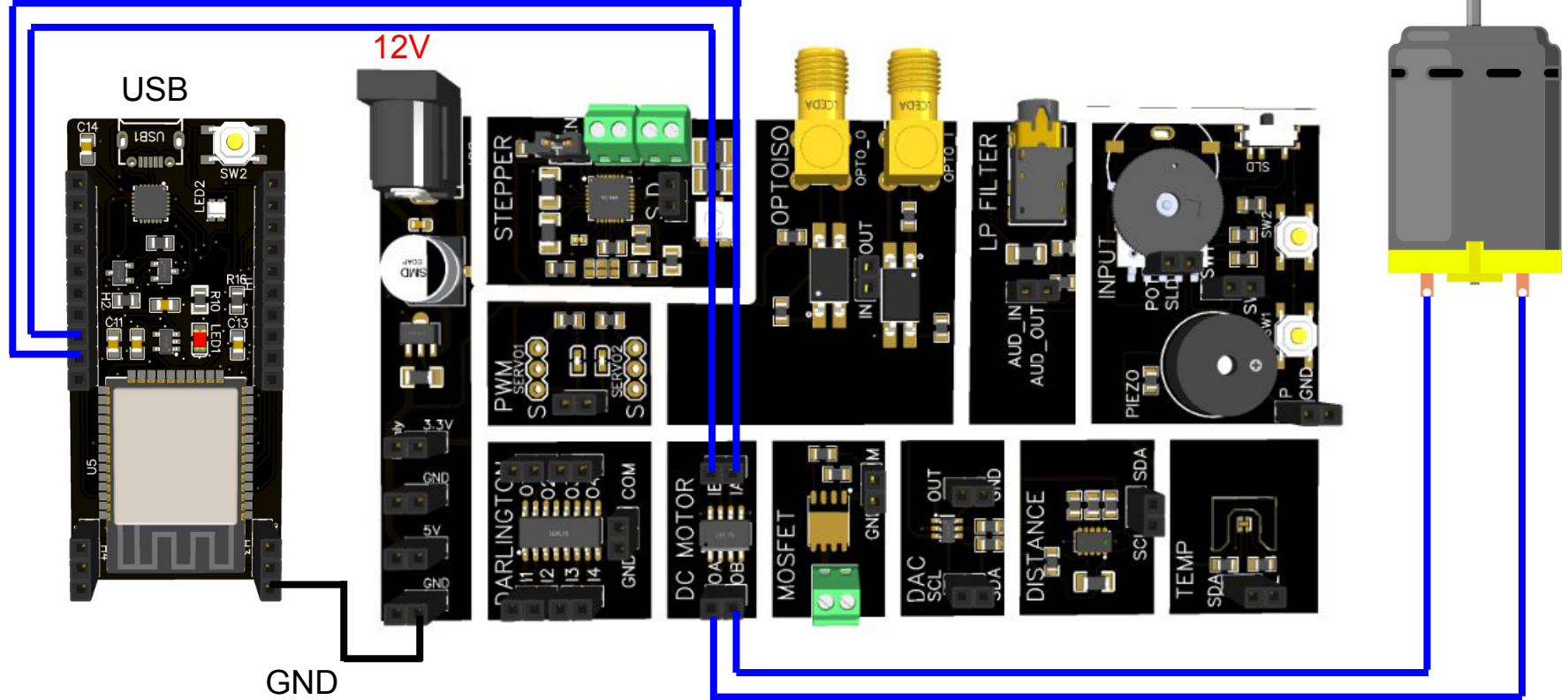

Servo motors

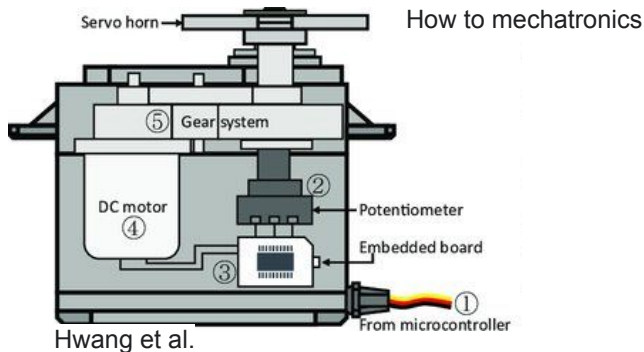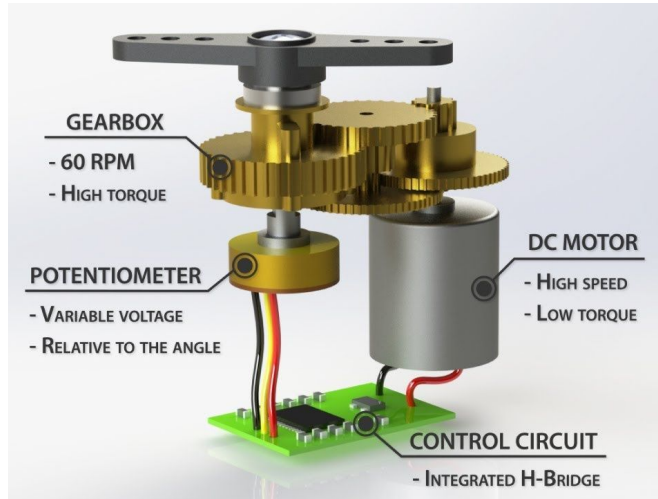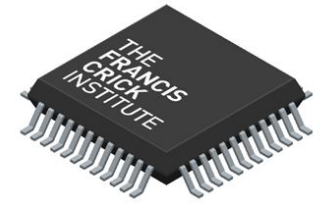

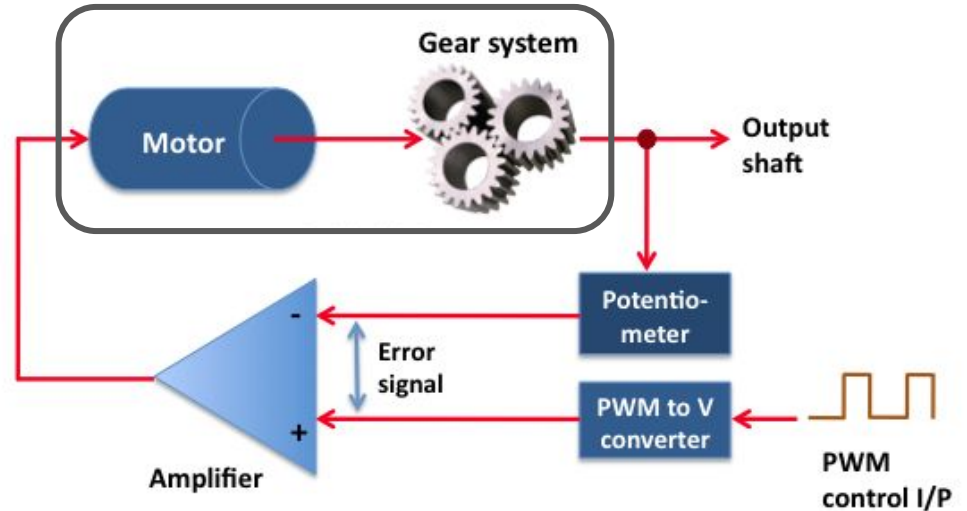
Position control system embedded on the motor








Embedded lab

Servo motor control (Example 304)

GPIO 15 connected to S pin

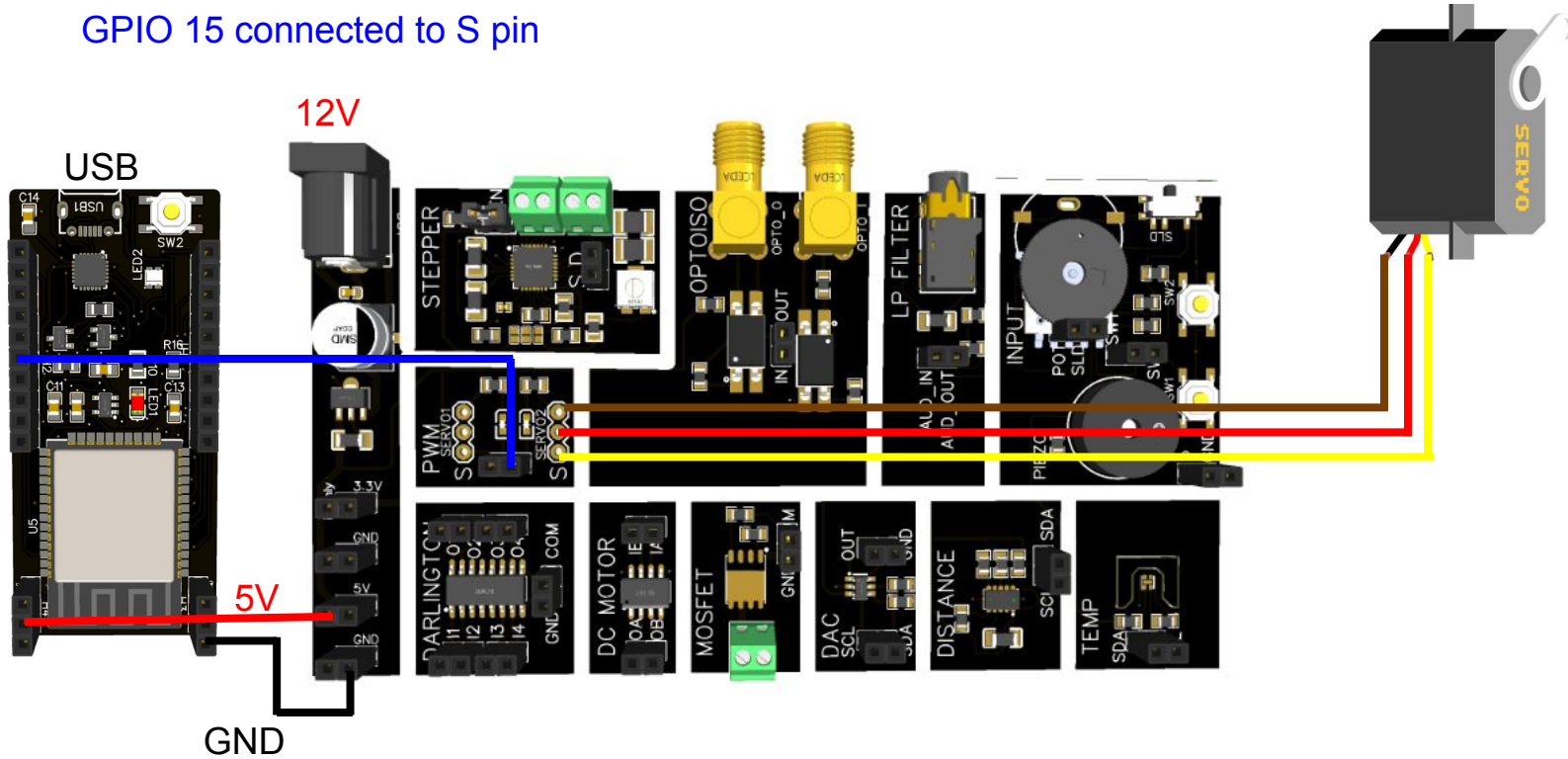


Stepper motors

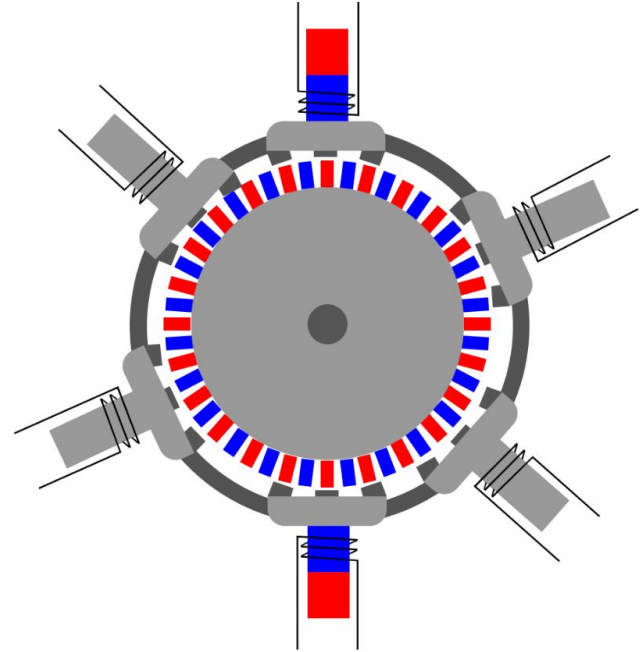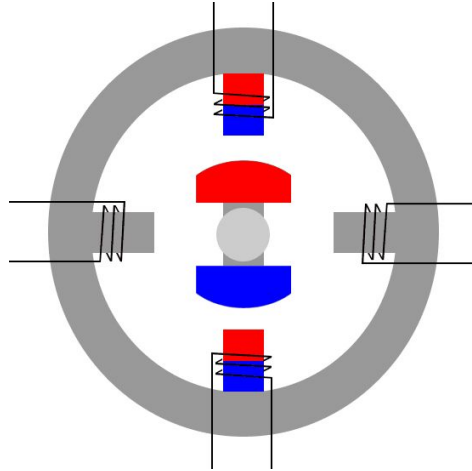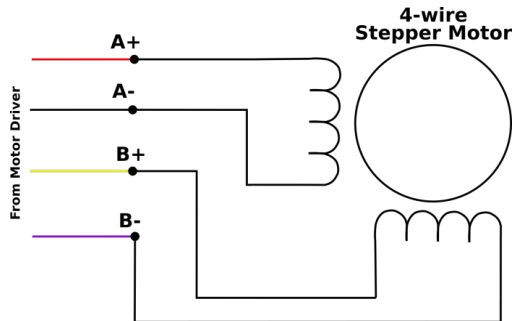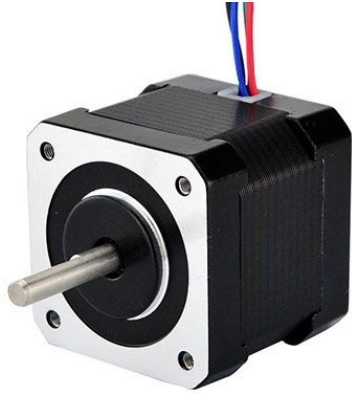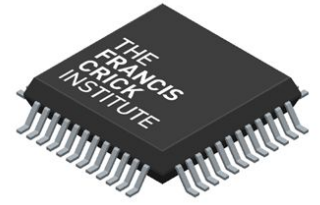


DrufelCNC

Stepper motor control (Examples on 305)

Step and Dir pin (GPIO 18 & 19)

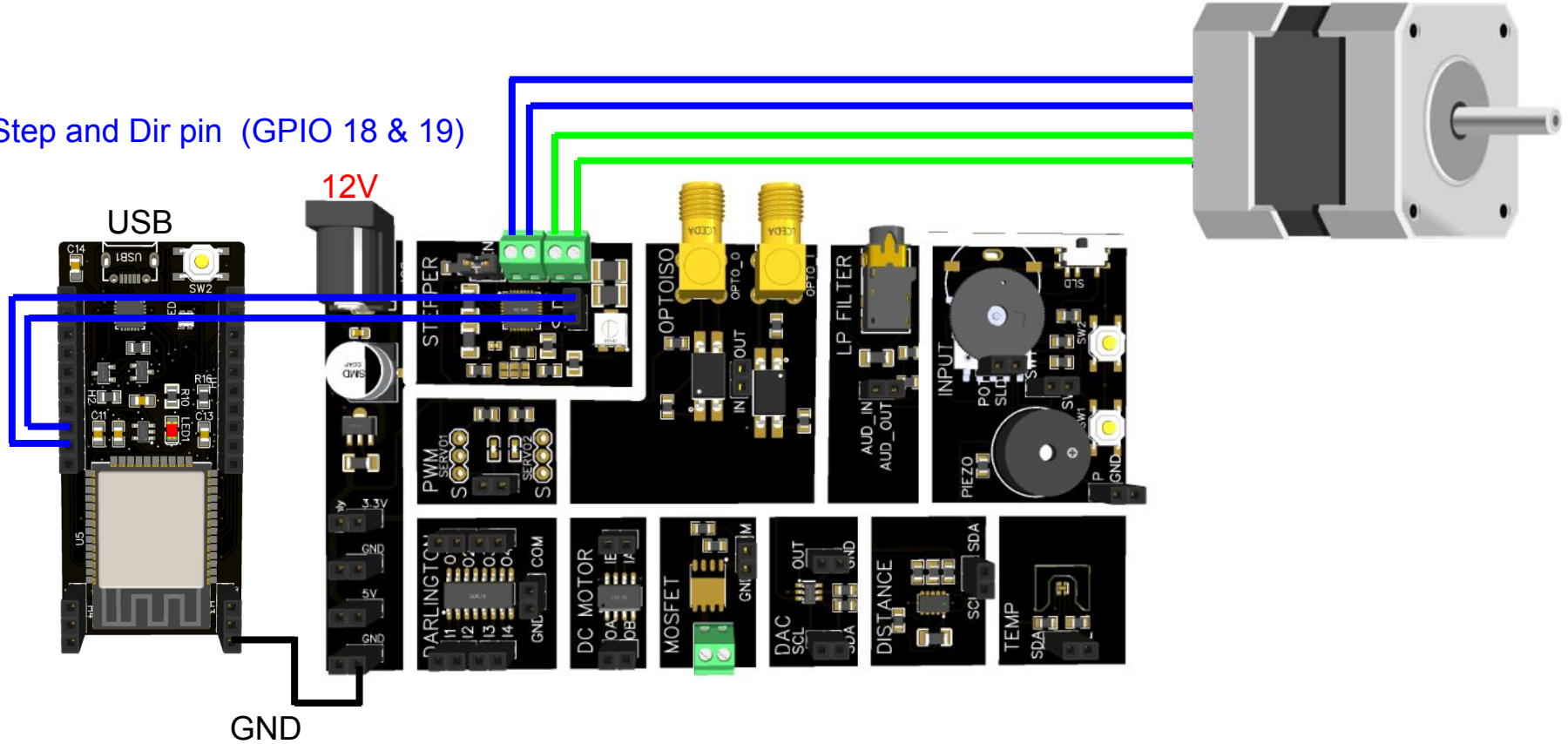

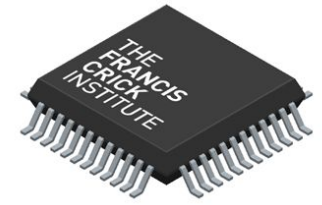
Stepper motors: microstepping and acceleration



MS1	MS2	MS3	Microstep Resolution
Low	Low	Low	Full step
High	Low	Low	Half step
Low	High	Low	Quarter step
High	High	Low	Eighth step
High	High	High	Sixteenth step


Pololu

Figure 2-6. Speed profile vs. stepper motor pulses/speed

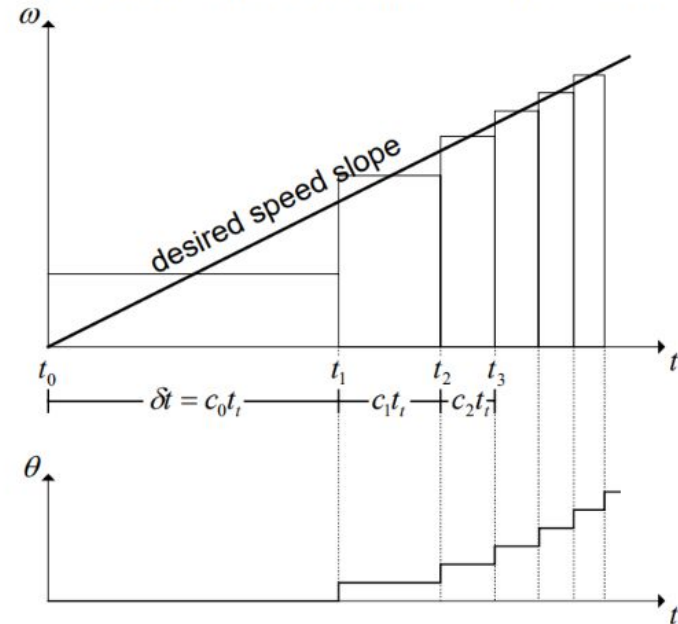

Atmel (AVR): “Linear speed control of stepper motors”

Proposed exercises

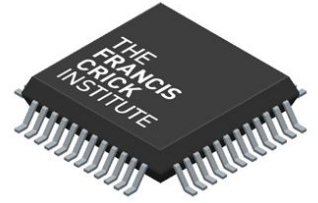




Use the Piezo as a user input

Control the LED brightness using the potentiometer


Control the DC motor speed using the potentiometer and the direction using one switch

Control the position of a stepper using a potentiometer and the same but having two/three velocities selected with a button or direction changed with a button.

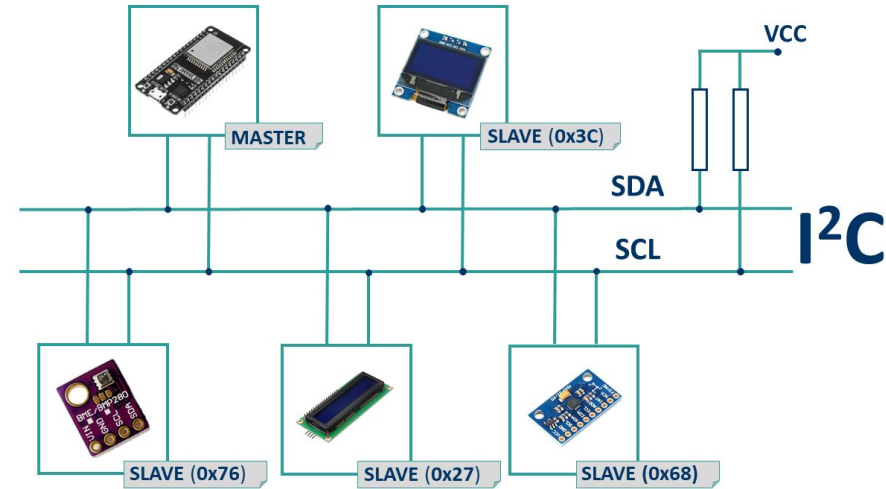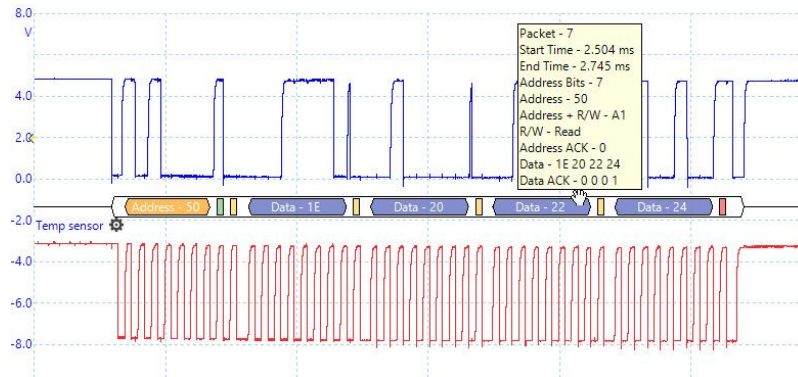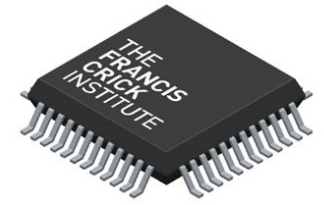I²C (Inter-Integrated Circuit, eye-squared-C)



Our Sensors

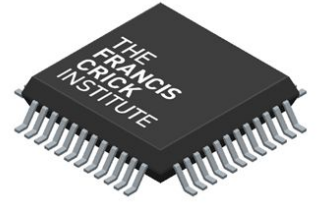

- **SHT4x** 4th Generation, High-Accuracy, Ultra-Low-Power, 16-bit Relative Humidity and Temperature Sensor
- **VL53L0X** Time-of-Flight Ranging Sensor